



Department of Computer Science & Engineering

Course No : CSE3110
Course Title : Digital System Design

Experiment No : 01
Experiment Name : ALU Implementation

Date of Submission : 3 December 2022
Submitted to : Md Raqibul Hasan & Anika Rahman

Submitted by –

Group No : 03(A2)
Name : Aurprita Mahmood
Sumaiya Shejin
Ziyan Shirin Raha
Meherin Sultana
Yasir Arafah Prince
Id : 20200104035, 20200104043,
20200104033, 20200104036,
20200104042
Section : A

Problem Statement: The problem statement is given below:-

S_2	S_1	S_0	Output	Function
1	0	1	$A_i - B_i$	Subtract
1	0	0	$A_i + 1 + 1$	Transfer A with carry
0	0	1	$A_i - 1$	Decrement A
0	0	0	$A_i - B_i - 1$	Subtract with Borrow
1	1	X	A_i'	Complement A
0	1	X	$A_i \cdot B_i$	AND

Introduction: The main purpose of this experiment is to design a ALU (Arithmetic and Logic Unit). Our ALU is 4 bit. This combinational circuit named ALU performs important functions like arithmetic and logic operators. Generating functions will be the goal of our experiment. For generating the function at first we will have to derive equation from the table given above using the selector bits for three inputs. After the k-map we have to simplify the equation then with the help of the software named proteus we will implement these functions. Thus the ALU will generate the output of the given functions.

Function Table: The function table is given below :-

S_2	S_1	S_0	X_i	Y_i	Z_i	Z_0/cin	Output
0	0	0	A_i	\bar{B}_i	C_i	0	$A_i - B_i - 1$
0	0	1	A_i	All 1	C_i	0	$A_i - 1$
0	1	0	$A_i + \bar{B}_i$	\bar{B}_i	0	0	$A_i \cdot B_i$
0	1	1	$A_i + \bar{B}_i$	\bar{B}_i	0	0	$A_i \cdot B_i$
1	0	0	A_i	All 1	C_i	1	$A_i + 1 + 1$
1	0	1	A_i	\bar{B}_i	C_i	1	$A_i - B_i$
1	1	0	\bar{A}_i	0	0	0	A_i'
1	1	1	\bar{A}_i	0	0	0	A_i'

K-map: For Z_0 ,

	$\bar{S}_1 \bar{S}_0$	$\bar{S}_1 S_0$	$S_1 S_0$	$S_1 \bar{S}_0$
\bar{S}_2	0	0	0	0
S_2	1	1	0	0

$$Z_0 = S_2 \bar{S}_1 C_i$$

For Z_i ,

	$\bar{S}_1 \bar{S}_0$	$\bar{S}_1 S_0$	$S_1 S_0$	$S_1 \bar{S}_0$
\bar{S}_2	C_i	C_i	0	0
S_2	C_i	C_i	0	0

$$Z_i = C_i \bar{S}_1$$

For Y_i ,

$s_2 \backslash s_1 s_0$	$\bar{s}_1 \bar{s}_0$	$\bar{s}_1 s_0$	$s_1 s_0$	$s_1 \bar{s}_0$
\bar{s}_2	\bar{B}_i	1	\bar{B}_i	\bar{B}_i
s_2	1	\bar{B}_i	0	0

$$\begin{aligned}
 Y_i &= \bar{s}_2 \bar{s}_0 \bar{B}_i + \bar{s}_2 \bar{s}_1 s_0 + \bar{s}_2 s_1 \bar{B}_i + s_2 \bar{s}_1 \bar{s}_0 + s_2 \bar{s}_1 s_0 \bar{B}_i \\
 &= \bar{s}_i (\bar{s}_2 s_0 + s_2 \bar{s}_0) + \bar{B}_i (\bar{s}_2 \bar{s}_0 + \bar{s}_2 s_1 + s_2 \bar{s}_1 s_0) \\
 &= \bar{s}_i (s_2 \oplus s_0) + \bar{B}_i (\bar{s}_2 \bar{s}_0 + \bar{s}_2 s_1 + s_2 \bar{s}_1 s_0)
 \end{aligned}$$

For X_i ,

$s_2 \backslash s_1 s_0$	$\bar{s}_1 \bar{s}_0$	$\bar{s}_1 s_0$	$s_1 s_0$	$s_1 \bar{s}_0$
\bar{s}_2	A_i	A_i	$A_i + \bar{B}_i$	$A_i + \bar{B}_i$
s_2	A_i	A_i	\bar{A}_i	\bar{A}_i

$$= A_i \bar{s}_1 + \bar{s}_2 s_1 (A_i + \bar{B}_i) + \bar{A}_i s_2 s_1$$

Result:

For subtract with borrow operation —

Selection			Input (A)				Input (B)				Output				
S ₂	S ₁	S ₀	A ₃	A ₂	A ₁	A ₀	B ₃	B ₂	B ₁	B ₀	Cout	F ₃	F ₂	F ₁	F ₀
			1	1	0	0	1	0	0	0	1	0	0	1	1
0	0	0	1	1	1	0	1	0	0	1	1	0	1	0	0
			1	0	0	1	0	1	1	1	1	0	0	0	1

For decrement operation —

Selection			Input (A)				Input (B)				Output				
S ₂	S ₁	S ₀	A ₃	A ₂	A ₁	A ₀	B ₃	B ₂	B ₁	B ₀	Cout	F ₃	F ₂	F ₁	F ₀
			0	1	1	1	0	1	0	0	1	0	1	1	0
0	0	1	1	1	0	1	0	1	1	0	1	1	1	0	0
			1	0	1	1	1	1	0	0	1	1	0	1	0

For AND operation —

Selection			Input (A)				Input (B)				Output				
S ₂	S ₁	S ₀	A ₃	A ₂	A ₁	A ₀	B ₃	B ₂	B ₁	B ₀	Cout	F ₃	F ₂	F ₁	F ₀
			1	1	0	1	1	1	0	0	0	1	1	0	0
0	1	X	0	1	1	1	1	1	0	1	0	0	1	0	1
			1	0	1	1	1	0	1	0	0	1	0	1	0

For transfer with carry operation:-


Selector			Input (A)				Input (B)				Output				
S ₂	S ₁	S ₀	A ₃	A ₂	A ₁	A ₀	B ₃	B ₂	B ₁	B ₀	Carry	F ₃	F ₂	F ₁	F ₀
			0	1	1	0	0	0	0	1	1	0	1	1	0
1	0	0	1	0	1	0	0	0	0	1	1	1	0	1	0
			0	0	1	0	0	0	0	1	1	0	0	1	1


For subtract operation:-

Selector			Input (A)				Input (B)				Output				
S ₂	S ₁	S ₀	A ₃	A ₂	A ₁	A ₀	B ₃	B ₂	B ₁	B ₀	Carry	F ₃	F ₂	F ₁	F ₀
			1	0	1	1	0	1	0	1	1	0	1	1	0
1	0	1	1	1	1	1	0	0	1	1	1	1	1	0	0
			0	1	0	1	0	1	0	0	1	0	0	0	1

For complement operation:-

Selector			Input (A)				Input (B)				Output				
S ₂	S ₁	S ₀	A ₃	A ₂	A ₁	A ₀	B ₃	B ₂	B ₁	B ₀	Carry	F ₃	F ₂	F ₁	F ₀
			1	0	1	0	0	0	0	0	0	0	1	0	1
1	1	X	0	0	1	1	0	0	0	0	0	1	1	0	0
			1	0	0	1	0	0	0	0	0	0	1	1	0

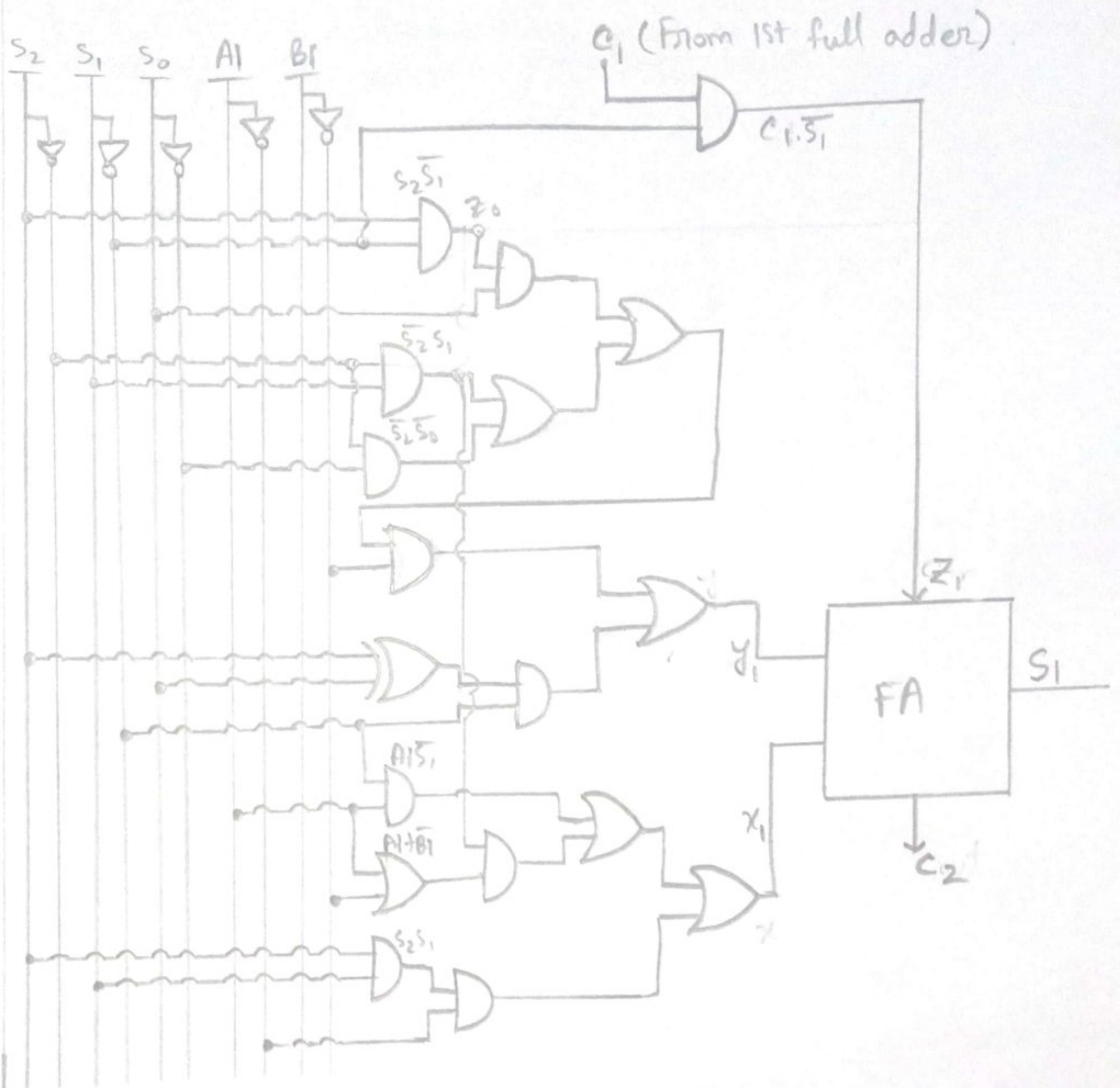

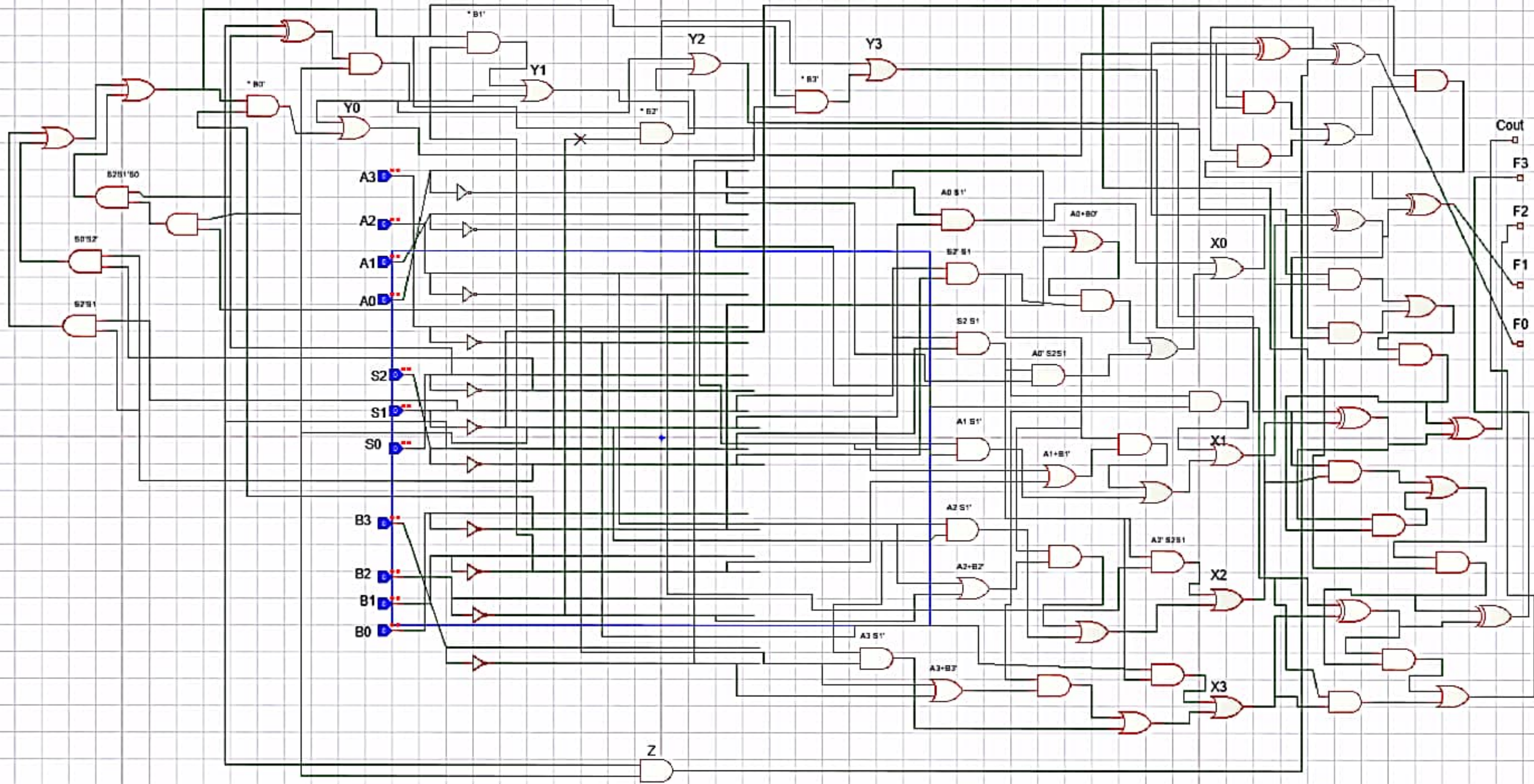

Conclusion: The proteus software that we use to execute the stimulation have some features, and on that account the instrumental errors occur. At first our ALU (Arithmetic and Logical Unit) was giving us some inaccurate results on outputs for logical operations however for some reason it was working accurately for our arithmetic operations. Thus we had to implement the circuit using direct equations without simplifying it and this time the functions were working correctly. But after practical implementation there might be an error in fact the IC's we use can be also become more prone to error.